

**Electrical Technician (Power Option) Level 6**  
**ENG/OS/PO/CC/03/6**  
**Apply Electrical Principles**  
**3 Hours**  
**March/April 2023**



**THE KENYA NATIONAL EXAMINATIONS COUNCIL**

**WRITTEN ASSESSMENT**

**3 HOURS**

**INSTRUCTIONS TO CANDIDATE**

*This paper consists of **TWO** sections **A** and **B**.*

*Answer **ALL** questions in section **A** and any **THREE** in section **B** in the answer booklet provided.*

*You are required to have a non-programmable calculator.*

*Marks for each question are indicated in brackets.*

*Answer the questions in **English**.*

**This paper consists of four (4) printed pages**

**Candidate should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.**

**SECTION A: (40 MARKS)**

Answer **all** questions in this section

1. State the SI units of: [2 Marks]
  - a) Charge;
  - b) Force.
2. List **two** types of electrical indicating instruments. [2 Marks]
3. A current of 10A flows through a heating element of an electric kettle for two minutes, find the quantity of electricity consumed. [2 Marks]
4. State Kirchoff's laws. [2Marks]
5. Determine the power dissipated by the coil of a d.c motor of resistance  $15 \Omega$  when a current of 1 A passes through it. [2 Marks]
6. A current of 1.2 A flows for 12 hours through a  $1 \text{ K}\Omega$  resistor. Calculate the energy consumed by the resistor. [3 Marks]
7. State **four** types of solar panels. [4 Marks]
8. Figure 1 shows the connection of an Anderson bridge for measuring the inductance L and resistance R of the coil. Find R and L, if balance is obtained when,  $R_4 = R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 500\Omega$ ,  $r = 100\Omega$  and  $C = 0.5 \mu\text{F}$ . [4Marks]

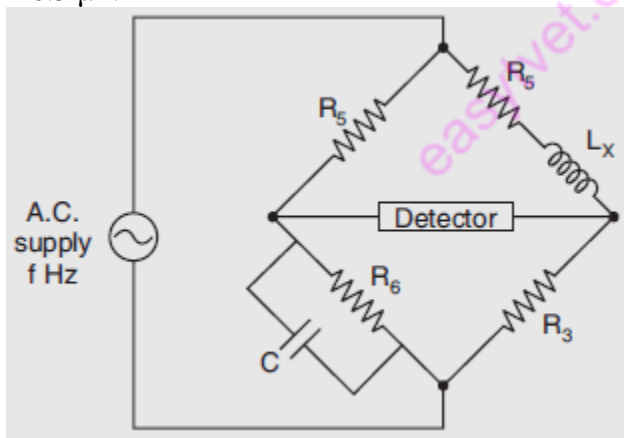


Figure 1.

9. Two brass plates are arranged horizontally, one 2 cm above the other and the lower plate is earthed. The plates are charged to a difference of potential of 6,000 volts. A drop of oil with an electric charge of  $1.6 \times 10^{-19} \text{ C}$  is in equilibrium between the plates so that it neither rises nor falls. Determine the mass of the drop. [4Marks]
10. With the aid of a diagram, differentiate between star and delta transformer connections. [2 Marks]
11. With reference to delta-connected system, state the relationships between the following:
  - i. line and phase currents;
  - ii. line and phase voltages. [2 Marks]
12. List the **three** wattmeter methods used for the measurements of power in a three-phase system. [3 Marks]
13. List **two** factors to consider while selecting an electrical protective device. [2 Marks]

14. State **two** reasons for balancing single-phase loads across a three-phase supply. [2 Marks]
15. Define the following terms with reference to earthing in an electrical installation:
- Current rating of a fuse;
  - Rated minimum fusing current. [4 Marks]

**SECTION B: (60 MARKS)**

*Answer **three** questions from this section.*

16. (a) (i) Explain **three** methods of correcting of low power factor. [6 marks]
- (ii) State **two** advantages of each of the methods mentioned in a(i) [6marks]
- (b) A 240 V supply feeds three 2 kW loads with power factors of 1, 0.7 and 0.3. Calculate the current at each power factor. [8 marks]
17. (a) List **three** importance for earthing. [3marks]
- (b) Identify **three** methods that can be used to achieve earthing of an installation. [6 marks]
- (c) Outline **three** earthing tests that should be carried out in a completed electrical installation. [4 marks]
- (d) Explain the operation of a current transformer. [3 marks]
- (e) List **four** parts of lightning protection system. [4Marks]
18. (a) An impedance  $Z_1 = (8 - j5) \Omega$  is in parallel with an impedance  $Z_2 = (3 + j7) \Omega$ . If 100 V are impressed on the parallel combination, find the branch currents  $I_1$ ,  $I_2$  and the resultant current.
- (i) Draw the corresponding phasor diagram showing each current and the voltage drop across each parameter.
- (ii) Calculate also the equivalent resistance, reactance and impedance of the whole circuit. [10 marks]
- (b) Point charges in air are located as follows:  $+ 5 \times 10^{-8} \text{ C}$  at (0, 0) meters,  $+ 4 \times 10^{-8} \text{ C}$  at (3, 0) meters and  $- 6 \times 10^{-8} \text{ C}$  at (0, 4) meters. Determine electric field intensity at (3, 4) meters. [5Marks]
19. (a) 250 kg of ice at  $- 20^\circ \text{C}$  is placed in a bunker to cool some vegetables. 12 hours later the ice has melted into water at  $5^\circ \text{C}$ . Determine the average rate of cooling in kJ/hr and Ton of refrigeration (TR) provided by the ice. [10 marks]

- (b) A refrigeration system produces 20 kg/hr of ice at 0°C from water at 12.5°C. Find the refrigeration effect per hour and TR. If it consumes 2 kW of energy to produce the ice, find the Coefficient of performance (COP). Take latent heat of solidification of water at 0°C as 335 kJ/kg and specific heat of water 4.19 kJ/kg °C. [10 marks]

**THIS IS THE LAST PRINTED PAGE.**